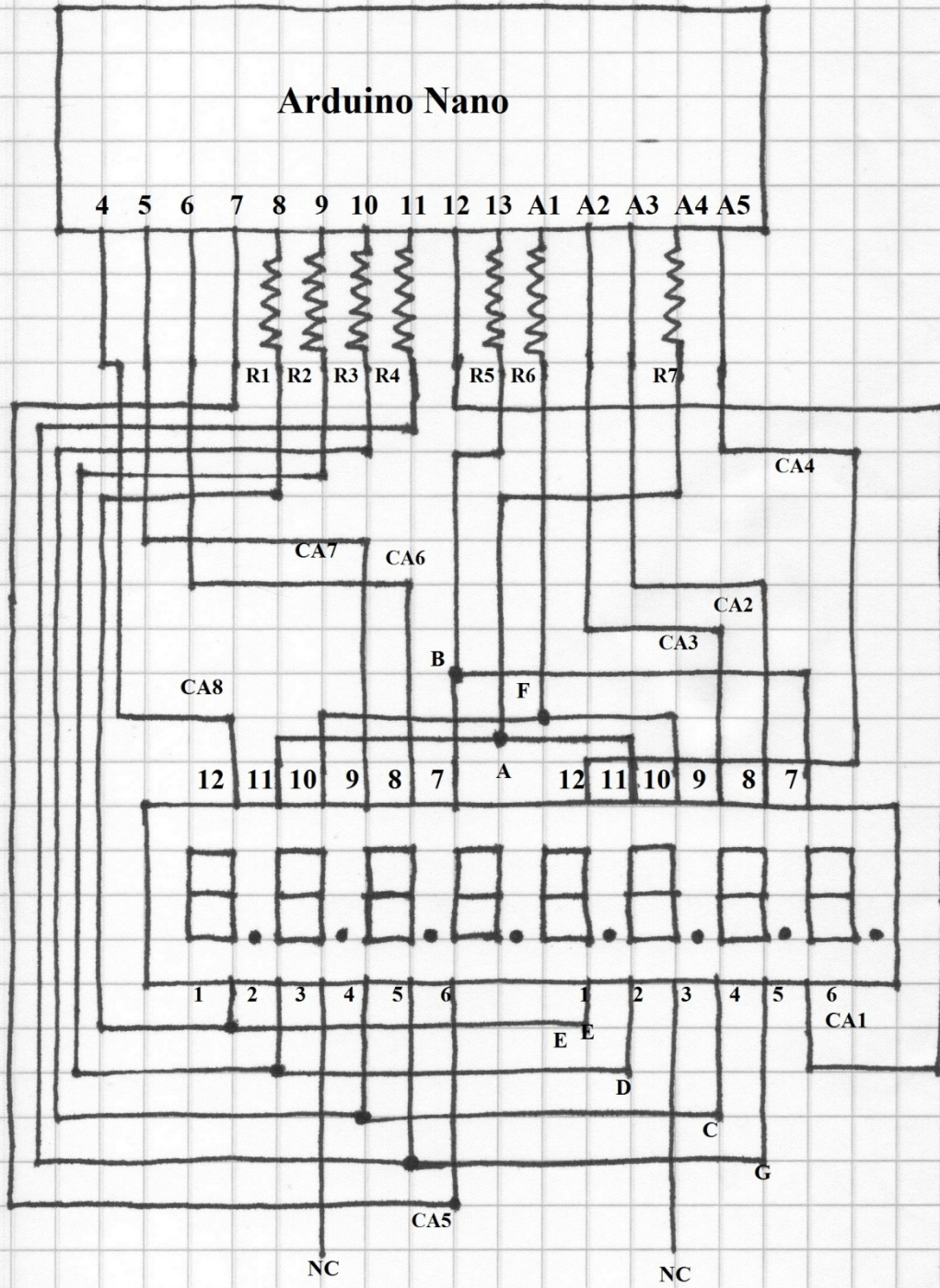


5 & 8 Digit Arduino Counter



2X4 BIT DISPLAY, Common Anode
R1-R7 = 220 Ohm, 1/4 Watt