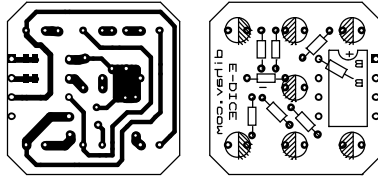


Electronic Dice

By Mohammad Yousefi (vahid_you2004@yahoo.com)

www.dihav.com



Print this page on an **A5 glossy paper** with a **laser printer without scaling**.

Microcontroller is a PIC12F675

The resistor on the IC is a 10K Ω and all other resistors are 470 Ω

Solder 10K Ω resistor on the back side

Solder a simple push button to the B terminals on the back side