

Portable Speaker Wiring Diagram

by Donny Terék



Parts list:

- 1 - 18650 Cells
- 2 - 3S BMS Board
- 3 - DC Input Jack
- 4 - 12V Latching LED Switch
- 5 - Momentary Switch
- 6 - Voltage Indicator
- 7 - Isolated Converter
- 8 - Amplifier
- 9 - 2X 1k Ohm Resistor
- 10 - WiFi/Bluetooth Audio Receiver
- 11 - Tactile Switch (for WiFi reset)
- 12 - AUX Input Jack

